

Laplace XFM

$$F(s) \equiv \int_0^{\infty} dt f(t) e^{-st} \quad \operatorname{Re}[s] > 0$$

s is analog of ω , but has no physical meaning

$$\text{inverse XFM: } f(t) = \frac{1}{2\pi i} \int_{\alpha-i\infty}^{\alpha+i\infty} ds \tilde{F}(s) e^{st}$$

ex: $\tilde{\delta}(t) = \int_0^{\infty} dt \delta(t) e^{-st} = 1$

$\frac{1}{t=0} \begin{matrix} \uparrow \\ \text{step} \end{matrix}$ $\tilde{u}(t) = \int_0^{\infty} dt u(t) e^{-st} = \frac{1}{s}$


$\widetilde{e^{-at}} = \int_0^{\infty} dt e^{-(s+at)} = \frac{1}{s+a}$

table

Convolution: $f(t) * g(t) = \int_0^t dt' f(t') g(t-t')$ (Laplace

$$\widetilde{[f * g]} = \tilde{f}(s) \cdot \tilde{g}(s)$$

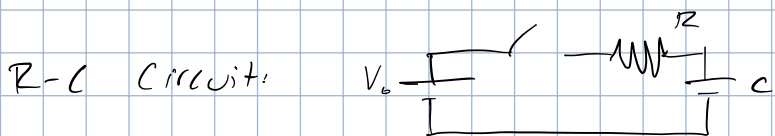Laplace often F^k 's that make Fourier XFM $\rightarrow \infty$



Usual Kirchhoff: V -drops $V = V_R + V_C = IR + \frac{Q}{C}$

$$\dot{Q} = I \rightarrow \dot{V} = \dot{I}R + \frac{\dot{Q}}{C} = \dot{I}R + \frac{1}{C}I$$

one more feature of L.T.: $\widetilde{\dot{f}(t)} = s \tilde{f}(s) - f(0)$

$$\widetilde{\ddot{f}(t)} = s^2 \tilde{f}(s) - s f(0) - \dot{f}(0)$$

take L.T. $[\dot{V} = \dot{I}R + \frac{1}{C}I] = s\tilde{V} - V(0) = (s\tilde{I} - I(0))R + \frac{1}{C}\tilde{I}$

L.T. is linear $\widetilde{f+g} = \tilde{f} + \tilde{g}$, same for inverse

if $V(0) = 0$ & $I(0) = 0$, $s\tilde{V} = (sR + \frac{1}{C})\tilde{I}$

for sudden turn-on: $v(t) = V_0 \cdot U(t) \equiv \int_{t=0}^{V_0} \rightarrow \leftarrow$

$$V_0 s \hat{U} = (sR + \frac{1}{C}) \hat{I}$$


$$\hat{I}(s) = \frac{1}{sR + \frac{1}{C}} \cdot s V_0 \hat{U} = \frac{V_0}{sR + \frac{1}{C}} = \frac{V_0/R}{s + \frac{1}{RC}} = \frac{V_0}{R} \cdot \frac{1}{s + \frac{1}{RC}}$$

$$= \frac{V_0}{R} \cdot e^{-t/RC}$$

$$I(t) = \frac{V_0}{R} e^{-t/RC} \text{ for } t \geq 0$$

L7. Ohm's Law

LCR circuit:

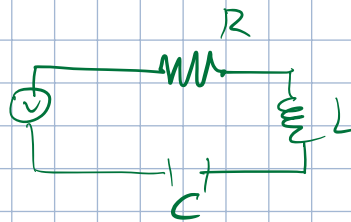

$$V = V_R + V_L + V_C$$

$$\hat{V} = \hat{V}_R + \hat{V}_L + \hat{V}_C$$

$$= \hat{I}R + \hat{I}L + \frac{d\hat{Q}}{dt}$$

$$= \hat{I}R + L \cdot (s\hat{I} - I(0)) + \frac{\hat{Q}}{C}$$

$$\hat{Q} = \hat{I} \quad \hat{Q} = s\hat{Q} - Q(0) = \hat{I}$$

$$\hat{V}_C = \frac{\hat{Q}}{sC} = \frac{\hat{I}}{sC}$$

$$\rightarrow \hat{V}_{\text{damps}} = \hat{I}R, sL\hat{I}, \frac{1}{sC}\hat{I}$$

$$\hat{V} = [R + sL + \frac{1}{sC}] \hat{I}$$

$$\hat{I} = \frac{1}{R + sL + \frac{1}{sC}} \cdot (V_0 \hat{U})$$

V is a switch

$$\hat{I} = \frac{V_0}{R + sL + \frac{1}{sC}} \cdot \frac{1}{s} = \frac{V_0/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{V_0/L}{\alpha} \left[\frac{1}{s+a} - \frac{1}{s+b} \right]$$

$$a+b = \frac{R}{L} \quad a \cdot b = \frac{1}{LC} \quad \alpha = b - a$$

$$a, b = -\frac{R}{2L} \pm i \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

↳ damping factor γ

$$\rightarrow b - a = -2i \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

Δ driving freq

$$I(t) = \frac{V_0/L}{-2i\Delta} \left[e^{-at} - e^{-bt} \right]$$

$$= \frac{V_0/L}{-2i\Delta} e^{-\gamma t} \left(e^{-i\Delta t} - e^{i\Delta t} \right)$$

$$= \frac{V_0}{\Delta L} e^{-\gamma t} \sin(\Delta t)$$